

KS3 Electricity and Magnetism Knowledge Organiser

Key Words

<b>potential difference</b>	The amount of push (energy) provided by the battery to a moving charge.
<b>current</b>	The flow of electric charge.
<b>resistance</b>	The measure of how difficult it is for a flow of charge to pass through a component.
<b>independent variable</b>	The variable you change in an investigation to see how it affects the dependent variable.
<b>dependent variable</b>	The variable you measure or observe.
<b>control variable</b>	A variable that could affect the dependent variable so must be kept the same.


Circuit Diagrams

Electrical circuits are often represented by **circuit diagrams**. They are simple and easy to interpret. **Circuit symbols** are used to represent the **components** used in a circuit.

<b>switch (open)</b>	
<b>switch (closed)</b>	
<b>bulb</b>	
<b>cell</b>	
<b>battery</b>	
<b>ammeter</b>	
<b>voltmeter</b>	
<b>resistor</b>	
<b>motor</b>	

Series Circuits

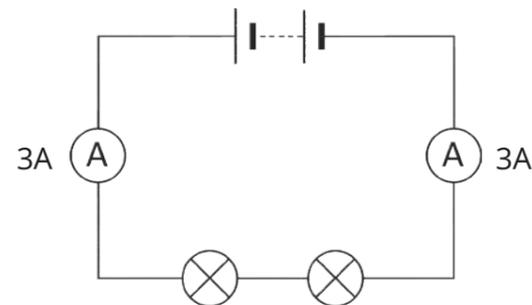In a series circuit, the components are connected end to end in a loop as shown in the diagram below. If one bulb breaks, none of the bulbs will be lit as the circuit is no longer complete.



The **current is the same** everywhere in a series circuit. It doesn't matter where you put the ammeter, it will always show the same reading. The more cells or batteries you add, the greater the current. Current is **not** used up.

Batteries

Batteries store **chemical energy** and transfer it as electric current in a circuit.


The potential difference of a battery tells us how much **energy** it provides to the components in the circuit.

Batteries contain an **electrolyte** and **two electrodes**. One of the electrodes is **positively charged** and the other is **negatively charged**. A chemical reaction between the two electrodes creates a flow of electrical energy to the circuit.



Parallel Circuits

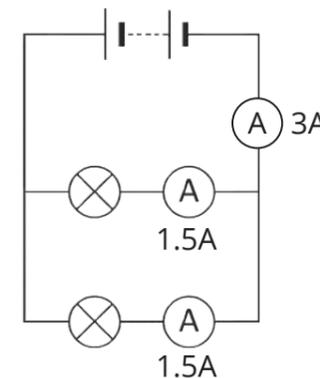
In a parallel circuit, the components are connected on separate branches as shown in the diagram below. This gives the current several different paths to flow down. If one bulb stops working, the other bulbs will remain lit as the circuit is still complete.



The **current is split** between the branches in a parallel circuit.

Modelling Circuits

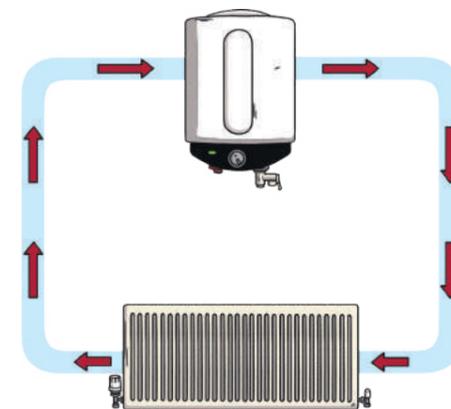
Scientists often use models to help them to explain difficult concepts. Some models are better than others.



In the boiler and radiator model, the pump pushes the water around the system. It does a similar job to a **battery** pushing the **charges** around a circuit. The pipes carry the flow of water around the system, like the **charge** flowing through wires in a circuit. The radiator is similar to a bulb because it transfers **energy** supplied by the system to the surroundings.


Current

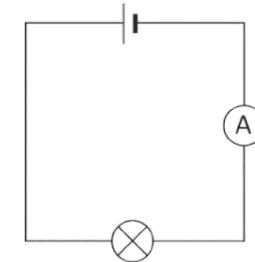Current is the flow of electrical charge around a circuit. The faster the flow of charge, the higher the current. Current is measured in **amps (A)** using an **ammeter**. An ammeter is connected in **series** with the component.



Potential Difference

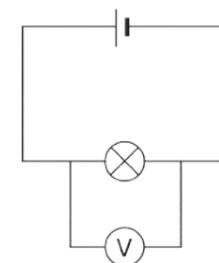Potential difference tells us how hard the battery 'pushes' the electrons around the circuit: the larger the potential difference, the bigger the 'push'. Potential difference is measured in **volts (V)** using a **voltmeter**. A voltmeter is connected in **parallel** with the component.



Resistance

Resistance is a measure of how difficult it is for the current to flow around a circuit.

The **higher the resistance**, the less current will flow around the circuit. The **lower the resistance**, the more current will flow around the circuit.

Resistance is measured in **ohms (Ω)**.

Resistance can be calculated using the equation:

$$\text{resistance } (\Omega) = \text{potential difference } (V) \div \text{current } (A)$$

KS3 Electricity and Magnetism Knowledge Organiser

**Resistance**

Factors that can affect the resistance through a wire include:

- temperature
- width of wire
- length of wire
- type of material

- As **temperature increases, resistance increases**. This is because the metal ions have more kinetic energy so they vibrate more, making it more difficult for electrons to flow.
- As the **width of the wire increases, resistance decreases** because there is more space for the electrons to flow.
- As the **length of the wire increases, resistance increases** because the electrons collide with more metal ions as they flow through the wire.
- Some materials are better **conductors** of electricity than others; they have **lower resistance** so they allow electrons to flow more easily.

**Magnetism**

Magnetism is a **non-contact force**. Magnetic materials can be magnetised or will be attracted to a magnet. There are three magnetic metals: **iron, nickel** and **cobalt**. Steel is also magnetic because it contains iron.

A bar magnet is a permanent magnet. It has a **north pole** and a **south pole**.

Like poles repel. This means that the two poles push each other away.




Opposite poles **attract**. This means that the invisible magnetic force between the magnets pulls the poles towards each other.



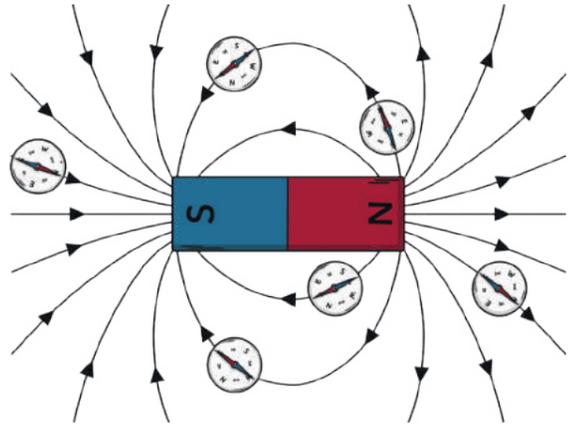**Magnetic Field Lines**


The magnetic field around a magnet can be shown as a series of lines around the magnet. The magnetic field lines can be plotted using a plotting compass.

The compass will always point towards to the south pole, wherever the compass is placed near the magnet. The arrows show the direction of the magnetic field.



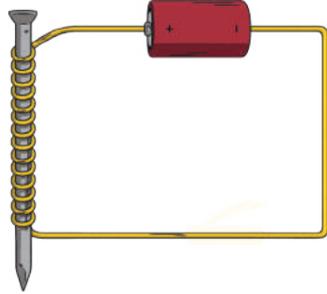**Electromagnets**

When electrical charge flows in a wire, a magnetic field is created around the wire. The larger the current, the stronger the electromagnet. The strength of the magnetic field can be increased by wrapping the wire around a magnetic material, such as iron.



The strength of an electromagnet can be changed by changing the number of coils of wire around the iron core. This can be measured by counting the number of paperclips that become attracted to the electromagnet.

**Independent variable** – number of coils of wire  
**Dependent variable** – number of paperclips picked up  
**Control variables** – current supplied to the circuit, core material, width of wire, length of wire, potential difference of the battery or power pack


The **greater the number of coils, the stronger the electromagnet** and the more paperclips it will pick up.

Electromagnets are useful because they can be switched on and off. This makes them suitable for sorting scrap metal at a recycling centre.

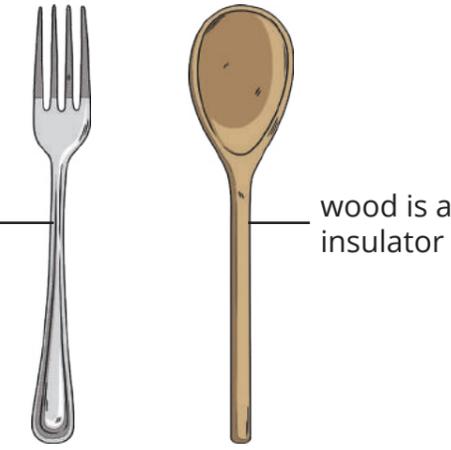**Resistance**

**Conductors** have **low resistance** so they allow current to pass through them easily.


**Insulators** have **high resistance** so it is difficult for current to flow through them.



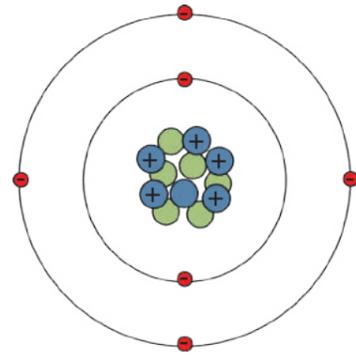**Atomic Structure**

There are two types of charge: positive (+) and negative (-).

All objects are made up of atoms. Atoms are made up of three different types of particle: a positive particle (**proton**), a negative particle (**electron**) and a particle with no charge (**neutron**). Atoms contain an equal number of protons and electrons. The number of positive and negative charges are balanced so an atom has **no overall charge**.



- electron
- ⊕ proton
- neutron

**Static Electricity**

Static electricity occurs when a material either loses or gains **electrons**. Electrons are negatively charged, so objects that **lose** electrons become **positively charged** overall, while objects that **gain** electrons become **negatively charged** overall.



When a polythene strip is rubbed with a cloth, electrons move from the cloth to the strip. The strip becomes negatively charged and the cloth becomes positively charged.



When you rub a balloon against your hair, electrons are transferred from your hair to the balloon. The balloon and your hair have opposite charges so your hair is attracted to the balloon, making it stand on end.



KS3 Electricity and Magnetism (Foundation) **Revision Mat**

**a** Draw a line from the name of each component to the correct circuit symbol.

ammeter	
battery	
bulb	
cell	
switch (open)	
voltmeter	

**b** Write down the unit of measurement for:

current \_\_\_\_\_

resistance \_\_\_\_\_

potential difference \_\_\_\_\_

What are the following components used to measure in a circuit?

ammeter \_\_\_\_\_

voltmeter \_\_\_\_\_

Complete the equation used to calculate resistance.

resistance = \_\_\_\_\_ ÷ \_\_\_\_\_

**c** Give the key word from its definition.

The flow of electric charge. \_\_\_\_\_

A material that has low resistance and allows current to flow through it easily. \_\_\_\_\_

A material that has high resistance and does not allow current to flow through it. \_\_\_\_\_

The amount of push (energy) provided by the battery to a moving charge. \_\_\_\_\_

A measure of how difficult it is for a flow of charge to pass through a component. \_\_\_\_\_


**d** Complete the sentences to describe the difference between series and parallel circuits. Choose answers from the box.

blows branches complete series parallel current

In a \_\_\_\_\_ circuit, the components are connected end to end in a loop. If one bulb breaks, none of the bulbs will light because the circuit is no longer \_\_\_\_\_.

In a \_\_\_\_\_ circuit, the components are connected on separate \_\_\_\_\_. This gives the \_\_\_\_\_ several different paths for it to flow around. If one bulb \_\_\_\_\_, the other bulbs will remain lit as the circuit is still complete.


**e** For each of the following circuits, predict whether the bulb will light and explain why.

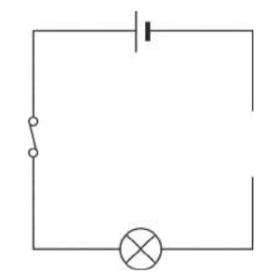**Circuit A** 

The bulb will/will not light because \_\_\_\_\_

\_\_\_\_\_


\_\_\_\_\_

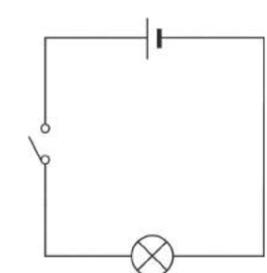**Circuit B** 

The bulb will/will not light because \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

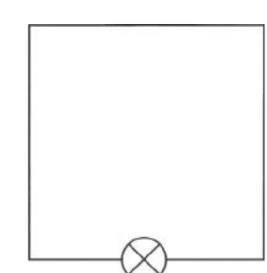**Circuit C** 

The bulb will/will not light because \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

**f** Match the name of each variable with the correct definition.

independent variable	This is a variable that must be kept the same.
dependent variable	This is the variable that you change or select the values for.
control variable	This is the variable that is measured in the investigation.

**g** Draw a series circuit containing one bulb, a battery, an ammeter and a switch.

**h** Draw a parallel circuit containing two bulbs, a battery and a switch that would allow both bulbs to be turned on.


KS3 Electricity and Magnetism (Foundation) Revision Mat

Complete the sentences.  
Choose answers from the box.

- |          |           |        |           |
|----------|-----------|--------|-----------|
| ammeter  | amps      | charge | electrons |
| parallel | voltmeter | volts  | series    |


Potential difference tells us how hard a battery pushes the \_\_\_\_\_ around a circuit: the higher the potential difference, the bigger the push.

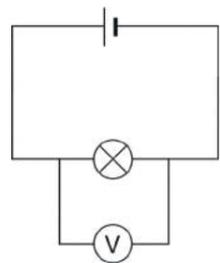Potential difference is measured in \_\_\_\_\_ using a \_\_\_\_\_ connected in \_\_\_\_\_ with the component.



Current is the flow of \_\_\_\_\_ around a circuit. The higher the current, the faster the electrons move.

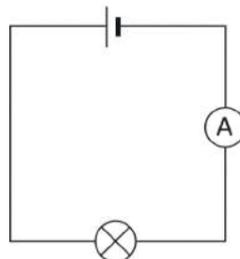Current is measured in \_\_\_\_\_ using an \_\_\_\_\_ connected in \_\_\_\_\_ with the component.



Tick the correct box to show if each statement is true or false.

- |   |                          |                          |
|---|--------------------------|--------------------------|
|   | <b>True</b>              | <b>False</b>             |
| All metals are magnetic.                        | <input type="checkbox"/> | <input type="checkbox"/> |
| All magnets have a north pole and a south pole. | <input type="checkbox"/> | <input type="checkbox"/> |
| The Earth has its own magnetic field.           | <input type="checkbox"/> | <input type="checkbox"/> |
| Opposite poles repel.                           | <input type="checkbox"/> | <input type="checkbox"/> |

Circle **three** magnetic metals in the list below.

- |           |        |        |
|-----------|--------|--------|
| aluminium | cobalt | copper |
| gold      | iron   | nickel |

Tick the correct box to show if each statement is true or false.

- |   |                          |                          |
|---|--------------------------|--------------------------|
|   | <b>True</b>              | <b>False</b>             |
| An atom has an equal number of protons and electrons.         | <input type="checkbox"/> | <input type="checkbox"/> |
| An atom has an overall positive charge.                       | <input type="checkbox"/> | <input type="checkbox"/> |
| Neutrons are negatively charged.                              | <input type="checkbox"/> | <input type="checkbox"/> |
| If a material gains electrons, it becomes positively charged. | <input type="checkbox"/> | <input type="checkbox"/> |

Explain why a person's hair stands on end if they touch the dome of a Van de Graaff generator.

\_\_\_\_\_


\_\_\_\_\_

\_\_\_\_\_

Label the diagram of an atom.

Choose answers from the box.

- |          |         |        |
|----------|---------|--------|
| electron | neutron | proton |
|----------|---------|--------|

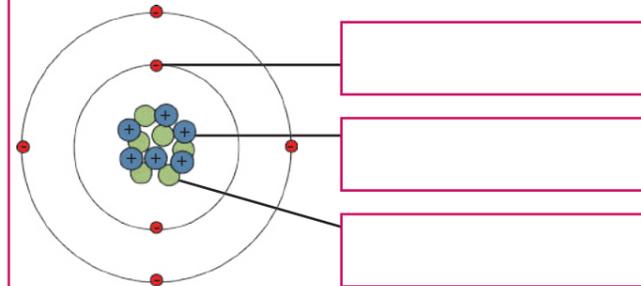

Match the name of each subatomic particle to its charge.

- |          |    |
|----------|----|
| electron | +1 |
| neutron  | 0  |
| proton   | -1 |

Complete the sentences.

Choose answers from the box.


- |       |               |        |
|-------|---------------|--------|
| coils | electromagnet | less   |
| more  | stronger      | weaker |

The strength of an \_\_\_\_\_ can be changed by changing the number of \_\_\_\_\_ of wire around an iron core.

The greater the number of coils, the \_\_\_\_\_ the electromagnet. The stronger the electromagnet, the \_\_\_\_\_ paperclips it will pick up.

Use the key words to explain what the diagram below shows.

- |               |
|---------------|
| current       |
| iron core     |
| electromagnet |
| coil of wire  |

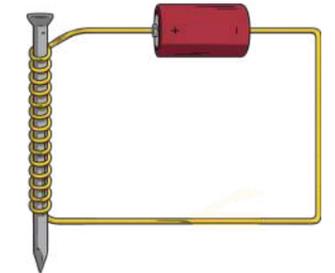

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Identify the variables in the electromagnet investigation.

independent variable

dependent variable

control variable

Complete the table.

Length of wire (cm)	Potential Difference (V)	Current (A)	Resistance (Ω)
30	10	5	
60	10	2	

Describe how the length of a wire affects its resistance.

\_\_\_\_\_

\_\_\_\_\_